
UM-SJTU JOINT INSTITUTE
PHYSICS LABORATORY
(VP 241)

LABORATORY REPORT

EXERCISE 5

RC, RL, AND RLC CIRCUITS

Name: Weikai Zhou

ID: 518021911039

Group: 8

Name: Yingtao Zou

ID: 518370910069

Group: 8

Date: 15 November 2019

1. Introduction [1]

1.1. Objectives

- Try to understand the physics of alternating-current circuits, in particular the processes of charging/discharging of capacitors, the phenomenon of electromagnetic induction in inductive elements, and other dynamic processes in RC, RL, and RLC series circuits.
- Study methods for measuring the amplitude-frequency and the phase-frequency characteristics of RC, RL, and RLC series circuits.
- Try to find the resonance frequency of a RLC circuit as well as the quality factor of the circuit from the amplitude-frequency curve.

1.2. Theoretical background

The basic elements of electric circuits are resistors, capacitors, and inductors. *RC*, *RL*, *RLC* alternating-current (AC) circuits will display various features, including transient, steady state, and resonant behavior, based on the particular arrangement of these elements.

1.2.1. Transient processes in *RC*, *RL*, *RLC* series circuits

1.2.1.1. *RC* series circuits

One example of a transient process is the process of charging or discharging of the capacitor in a RC circuit. The figure below shows a *RC* series circuit in which a square-wave signal is used as the source signal (Figure 1).

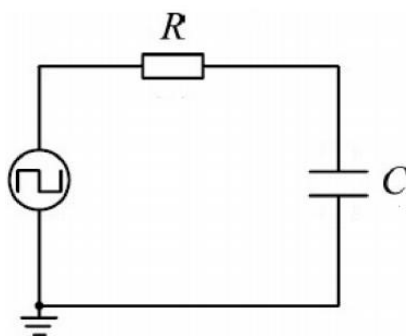


Figure 1. *RC* series circuit

We can see that the square-wave voltage is $U(t) = \varepsilon$ in the first half of the cycle. And it charges the capacitor. The square-wave voltage is zero in the second half of the cycle. And the capacitor discharges itself through the resistor. We can derive the loop equation (Kirchhoff's loop rule) for the charging process as

$$RC \frac{dU_C}{dt} + U_C = \varepsilon. \quad (1)$$

If the initial condition $U_C(t = 0) = 0$, the solution of Eq. (1) can be found as

$$U_C = \varepsilon \left(1 - e^{-\frac{t}{RC}} \right) \quad \text{and} \quad U_R = iR = \varepsilon e^{-\frac{t}{RC}}.$$

Then, we can find that the voltage across capacitor U_C increases exponentially with time t ,

while the voltage on the resistor U_R decreases exponentially with time t . The curves $U(t)$, $U_C(t)$ and $U_R(t)$ are shown in Figure 2.

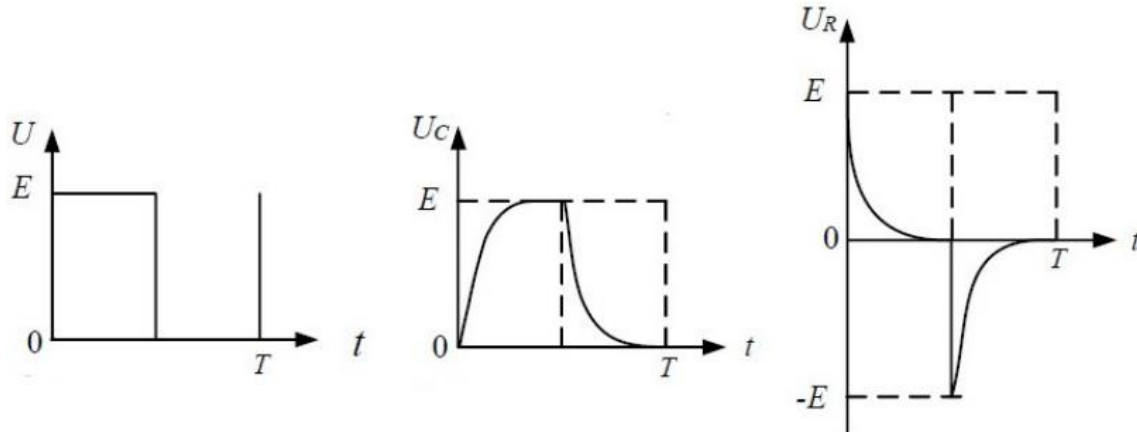


Figure 2. Charging/discharging curves for a RC series circuit

In the discharging process, the loop rule gives us

$$RC \frac{dU_C}{dt} + U_C = 0. \quad (2)$$

If the initial condition $U_C(t = 0) = \varepsilon$, the solution of Eq. (2) can be found as

$$U_C = \varepsilon e^{-\frac{t}{RC}} \quad \text{and} \quad U_R = iR = -\varepsilon e^{-\frac{t}{RC}},$$

where the magnitude of both U_C and U_R decrease exponentially with time. We call $RC = \tau$ the *time constant* and characterizes the dynamics of the transient process because it has the units of time. Another characteristics related to the time constant called the *half-life period* $T_{1/2}$ is easier to measure in experiments. It means the time needed for U_C to decrease to a half of the initial value (or increase to a half of the terminal value). And we may use it to characterize the dynamics of the transient process. In the process with exponential dynamics discussed above, both quantities are related by the equation that

$$T_{1/2} = \tau \ln 2 \approx 0.693\tau.$$

1.2.1.2. RL series circuit

We can carry a similar analysis for RL series circuit and get that

$$\tau = \frac{L}{R} \quad \text{and} \quad T_{1/2} = \frac{L}{R} \ln 2$$

1.2.1.3. RLC series circuit

When a power source is suddenly plugged into a RLC circuit, the voltage across the capacitor satisfies the differential equation that based on the loop rule

$$LC \frac{d^2 U_C}{dt^2} + RC \frac{dU_C}{dt} + U_C = \varepsilon. \quad (3)$$

If we divide both sides of equation by LC and introducing the symbols that

$$\beta = \frac{R}{2L} \quad \text{and} \quad \omega_0 = \frac{1}{\sqrt{LC}}, \quad (4)$$

we can simplify Eq. (3) as

$$\frac{d^2 U_C}{dt^2} + 2\beta \frac{dU_C}{dt} + \omega_0^2 U_C = \omega_0^2 \varepsilon. \quad (5)$$

We should note that Eq. (5) is an inhomogeneous differential equation and it is mathematically equivalent to the equation of motion of a damped harmonic oscillator with a constant driving force. If β is the damping coefficient and ω_0 is the natural angular frequency, the complementary homogeneous equation is fully analogous to the equation of motion of a damped harmonic oscillator. Moreover, after a specific solution to the inhomogeneous equation is found, a unique solution to the initial value problem consisting of Eq. (5) and the initial conditions can be found as

$$U_C(t = 0) = 0 \quad \text{and} \quad \left. \frac{dU_C}{dt} \right|_{t=0} = 0. \quad (6)$$

There are 3 regimes, depending on the relation between β and ω_0 for mechanical oscillations, as implied by the solution of the complementary homogeneous equation:

- $\beta^2 < \omega_0^2$ (weak damping): the system is in the underdamped regime and the solution to the initial value problem is of the form:

$$U_C = \varepsilon - \varepsilon e^{-\beta t} \left(\cos \omega t + \frac{\beta}{\omega} \sin \omega t \right),$$

where $\omega = \sqrt{\omega_0^2 - \beta^2}$.

- $\beta^2 > \omega_0^2$ (strong damping): the system is in the overdamped regime with the solution of the form

$$U_C = \varepsilon - \frac{\varepsilon}{2\gamma} e^{-\beta t} [(\beta + \gamma)e^{\gamma t} - (\beta - \gamma)e^{-\gamma t}],$$

where $\omega = \sqrt{\beta^2 - \omega_0^2}$.

- $\beta^2 = \omega_0^2$: the system is in the critically damped with the solution of the form

$$U_C = \varepsilon - \varepsilon(1 + \beta t)e^{-\beta t}. \quad (7)$$

We will suddenly remove the power source ($\varepsilon = 0$) when the circuit reaches a steady state. The differential equation for the discharging process is similar to that of the charging process, and there are also three regimes of the process.

The discussion above is true for an ideal circuit and a step-signal source with zero internal resistance. However, during the experiment, we use a square-wave source with a small internal resistance as the ideal case. We need to remember that the period of the square-signal must be much greater than the time constant of the circuit. And we should also note that no matter what the regime is, the voltage across the capacitor will finally reach ε (Figure 3).

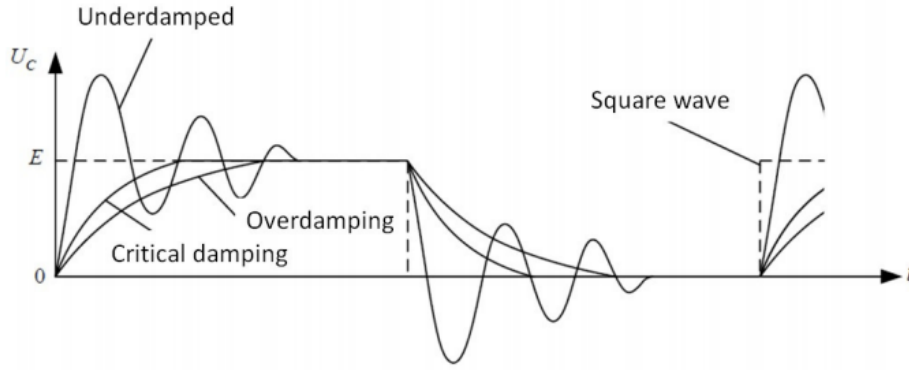


Figure 3. Three different regimes of transient processes in a RLC series circuit

1.2.2. RC , RL steady-state circuits

Usually, the amplitude and the phase of the voltage across the capacitor and the resistor will change with the frequency of the input voltage when a sinusoidal alternating input voltage is provided to a RC (or RL) series circuit. We can measure the voltage across the elements in the circuit for different input signal frequencies to obtain the amplitude vs. frequency relation and the phase vs. frequency relation.

$$\varphi = \tan^{-1} \frac{U_L}{U_R} = \tan^{-1} \frac{\omega L}{R}, \quad \varphi = \tan^{-1} \left(-\frac{U_C}{U_R} \right) = \tan^{-1} \left(-\frac{1}{\omega RC} \right).$$

1.2.3. RLC resonant circuit

1.2.3.1. RLC series circuit

The figure below shows a generic RLC series circuit (Figure 4).

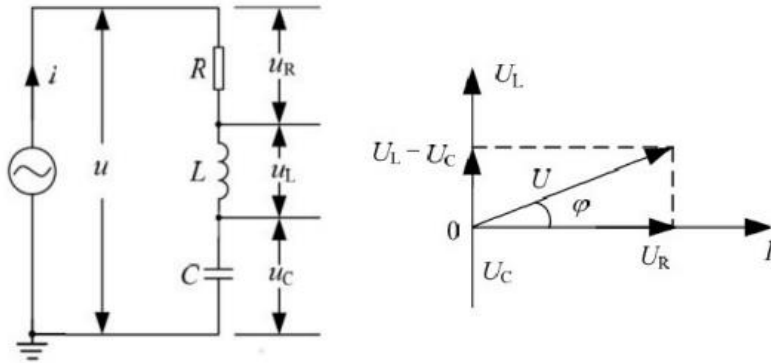


Figure 4. RLC series circuit

Using the phasors technique, we can easily calculate the impedance and the phase difference in the RLC circuit. The phase differences between the current and the voltages across the resistor, coil, and capacitor can be calculated as below if we represent the current I by a vector along the horizontal axis.

$$\varphi_R = 0, \quad \varphi_L = \frac{\pi}{2}, \quad \varphi_C = -\frac{\pi}{2}.$$

Then, the corresponding voltage amplitudes across the elements are

$$U_R = IZ = IR, \quad U_L = IZ_L = I\omega L, \quad U_C = IZ_C + \frac{I}{\omega C}.$$

Therefore, the voltage amplitude can be calculated as below

$$U = \sqrt{U_R^2 + (U_L - U_C)^2} \quad \text{or} \quad U = I \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}, \quad (8)$$

and the total impedance is

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}, \quad (9)$$

and the phase difference between the current and the voltage in the circuit is

$$\varphi = \tan^{-1} \left(\frac{U_L - U_C}{U_R} \right) = \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right).$$

1.2.3.2. Resonance

If the frequency of the input signal provided by the source satisfies the condition that

$$\omega_0 L = \frac{1}{\omega_0 C}, \quad \text{or, equivalently,} \quad \omega_0 = \frac{1}{\sqrt{LC}},$$

the total impedance will reach a minimum, $Z_0 = R$. We should pay attention that the resistance R in a real circuit includes the internal resistance and all kinds of alternating-current power losses, so its actual value will be greater than the theoretical one.

We say the circuit is at resonance if the current reaches its maximum, $I_m = U/R$. The frequency

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}},$$

at which the resonance phenomenon occurs, is called the *resonance frequency*.

The generic shapes of the total impedance Z , the current I , and the phase difference $\varphi = \varphi_u - \varphi_i$ are shown in Figure 5, and we can find that they are all frequency dependent.

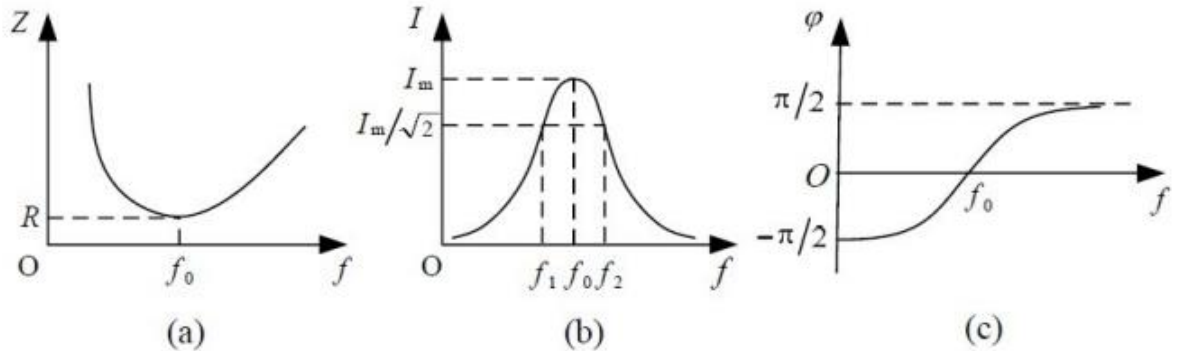


Figure 5. The impedance, the current and the phase difference as functions of the frequency for a RLC series circuit (generic sketches).

According to Eqs. (8) and (9), $\varphi < 0$ when the frequency is low ($f < f_0$, i.e. $1/\omega C > \omega L$). The total voltage lags behind the current and the circuit is said to be *capacitive* in this

case.

$\varphi = 0$ when the circuit is resonant ($f = f_0$, i. e. $1/\omega C = \omega L$). Moreover, the voltages across the capacitor and the inductor should be equal. The circuit is said to be *resistive*.

$\varphi > 0$ when the frequency is high ($f > f_0$, i. e. $1/\omega C < \omega L$). The total voltage leads the current, and the circuit is said to be *inductive* in this case.

1.2.3.3. Quality factor in resonant circuits

Using $I_m = U/R$, we can calculate the voltages across the resistor, the inductor, and the capacitor as

$$U_R = I_m R = U,$$

$$U_L = I_m Z_L = \frac{U}{R} \omega L,$$

$$U_C = I_m Z_C = \frac{U}{R \omega_0 C} = U_L,$$

respectively. The ratio of U_L (or U_C) to U is called the quality factor Q of a resonant circuit when the circuit is driven at the resonance frequency

$$Q = \frac{U_L}{U} = \frac{\omega_0 L}{R} \quad \text{or} \quad Q = \frac{U_C}{U} = \frac{1}{\omega_0 R C}.$$

If we fix the total voltage, the Q increases with the increase of U_L and U_C . The value of Q can be used to quantify the efficiency of resonant circuits.

The quality factor can also be found as

$$Q = \frac{f_0}{f_2 - f_1},$$

where f_1 and f_2 are two frequencies such that $I(f_1) = I(f_2) = I_m/\sqrt{2}$ (see Figure 5b).

2. Apparatus [1]

2.1. Experimental setup

The measurement consists of an oscilloscope, a signal generator, a wiring board, a digital multimeter, a variable resistor 2 k Ω (2 W), a fixed resistor 100 Ω (2 W), two inductors (10 mH and 33 mH) and two capacitors (0.47 μ F and 0.1 μ F).

2.2. Precision or uncertainty

R	0.01 Ω	$T_{\frac{1}{2}}$	0.001 μ s / 0.01 μ s
C	0.01 nF / 0.1 nF	L	0
f	0.001 Hz	U_R	0.02 V_{pp} / 0.002 V_{pp}
ε	0.001 V_{pp}		

Table 1. Precision or uncertainty

3. Measurement procedure [1]

3.1. *RC, RL* series circuit

- 3.1.1.** First, we choose a capacitor and an inductor to assemble a circuit with the fixed-resistance $100\ \Omega$ resistor. Then, we adjust the output frequency of the square-wave signal provided by the signal generator. We also observe the change of the waveform when the time constant is smaller or greater than the period of the square-wave. We should choose the frequency that allows the capacitor to fully charge/discharge. Besides, we should use the **PRINT** function of the oscilloscope to store the waveforms.
- 3.1.2.** Then, we should adjust display parameters of the oscilloscope and measure $T_{1/2}$ for the studied circuits. And we should calculate the time constant and compare it with the theoretical value. We should keep in mind that in order to find the time constant accurately, only one period should be displayed on the oscilloscope screen.

3.2. *RLC* series circuit

- 3.2.1.** First, we choose a capacitor and an inductor to assemble a *RLC* series circuit with the variable resistor. Then, we observe the waveform of the capacitor voltage in the underdamped, critically damped, and overdamped regimes. We should use the **PRINT** function of the oscilloscope to store the waveforms.
- 3.2.2.** Then, we should adjust the variable resistor to the critically damped regime. According to the definition of the half-life period $T_{1/2}$, we have $\beta T_{1/2} = 1.68$. By finding the value of $T_{1/2}$, the time constant can be found as $\tau = 1/\beta = T_{1/2}/1.68$. We also need to compare the result with the theoretical value.

3.3. *RLC* resonant circuit

We should apply a sinusoidal input voltage U_i to the *RLC* series circuit, change the frequency, then observe the change of the voltage U_R for a fixed resistor R , as well as the phase difference between U_R and U_i . We then need to measure how U_R changes with U_i and calculate the phase difference according to Figure 4. After that, we should plot the graphs I/I_m vs. f/f_0 and φ vs. f/f_0 . Finally, we should estimate the resonance frequency and calculate the quality factor Q .

4. Results

4.1. *RC, RL* series circuit

4.1.1. *RC* series circuit

According to the procedure described in 3.1., we can get the table below (Table 2).

Resistance R	$99.64 [\Omega] \pm 0.01 [\Omega]$
Frequency f	$5.000000 [\text{kHz}] \pm 0.001 [\text{Hz}]$
Voltage ε	$4.000 [V_{pp}] \pm 0.001 [V_{pp}]$
Capacitance C	$101.21 [\text{nF}] \pm 0.01 [\text{nF}]$
Half-life period $T_{1/2}$	$7.000 [\mu\text{s}] \pm 0.001 [\mu\text{s}]$

Table 2. $T_{1/2}$ measurement data for a RC series circuit

And the figure below shows the waveform of RC series circuit to fully charge/discharge (Figure 6).

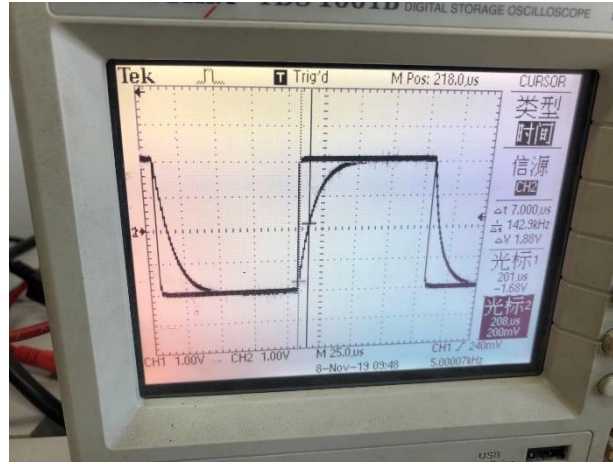


Figure 6. The waveform of RC series circuit to fully charge/discharge

Based on the experimental data of $T_{1/2}$, we can calculate the theoretical τ as

$$\tau_{\text{experimental}} = \frac{T_{1/2, \text{experimental}}}{\ln 2} = 1.00989 \times 10^{-5} \pm 1.4 \times 10^{-9} [\text{s}].$$

And we can calculate the theoretical value for τ as

$$\tau_{\text{theoretical}} = RC = 99.64 \times 101.21 \times 10^{-9} = 1.00846 \times 10^{-5} \pm 1.4 \times 10^{-9} [\text{s}].$$

The relative error between them is

$$\frac{|\tau_{\text{theoretical}} - \tau_{\text{experimental}}|}{\tau_{\text{theoretical}}} \times 100\% = 0.15\%,$$

which is very small.

4.1.2. RC series circuit

According to the procedure described in 3.1., we can get the table below (Table 3).

Resistance R	$99.64 [\Omega] \pm 0.01 [\Omega]$
Frequency f	$1.000000 [\text{kHz}] \pm 0.001 [\text{Hz}]$
Voltage ε	$4.000 [V_{pp}] \pm 0.001 [V_{pp}]$
Inductance L	$0.01 [\text{H}] \pm 0 [\text{H}]$
Half-life period $T_{1/2}$	$80.00 [\mu\text{s}] \pm 0.01 [\mu\text{s}]$

Table 3. $T_{1/2}$ measurement data for a RL series circuit

And the figure below shows the waveform of RL series circuit to fully charge/discharge (Figure 7).

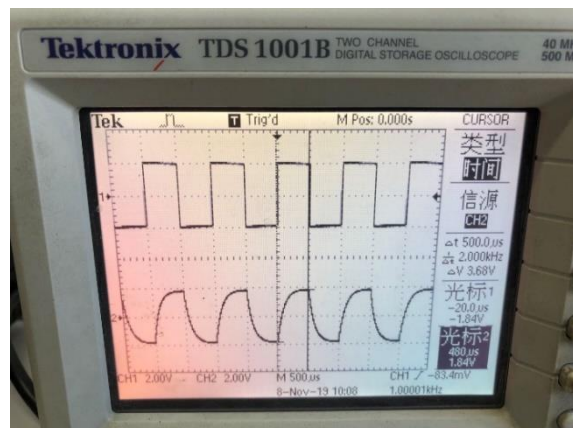


Figure 7. The waveform of RL series circuit to fully charge/discharge

Based on the experimental data of $T_{1/2}$, we can calculate the theoretical τ as

$$\tau_{experimental} = \frac{T_{1/2,experimental}}{\ln 2} = 1.154156 \times 10^{-4} \pm 1.4 \times 10^{-9} [s].$$

And we can calculate the theoretical value for τ as

$$\tau_{theoretical} = \frac{L}{R} = \frac{0.01}{99.64} = 1.004 \times 10^{-4} \pm 1.0 \times 10^{-6} [s].$$

The relative error between them is

$$\frac{|\tau_{theoretical} - \tau_{experimental}|}{\tau_{theoretical}} \times 100\% = 15.0\%,$$

which is relatively large. We may think that this is mainly because of precision of the device. When using the **CURSOR** function, it increases or decreases $10 \mu s$ each time I adjust it. And I failed to make it more precise. If I can make the device be more precise, for example, increase or decrease $1 \mu s$ each time, the result will be better. Besides, we do not measure the actual inductance of the inductor and just use the value labeled on it, which will also contribute to the error. Besides, the inductor is also not ideal.

4.2. RLC series circuit

According to the procedure in 3.2., we can get the table below (Table 4).

Inductance L	$0.01 [H] \pm 0 [H]$
Capacitance C	$101.21 [nF] \pm 0.01 [nF]$
Voltage ε	$4.000 [V_{pp}] \pm 0.001 [V_{pp}]$
Frequency f	$100.000000 [kHz] \pm 0.001 [Hz]$
βt	1.68
Half-life period $T_{1/2}$	$120.00 [\mu s] \pm 0.01 [\mu s]$

Table 4. $T_{1/2}$ measurement data for a critically damped RLC series circuit

Also, we recorded the figures for underdamped, critically damped and overdamped as shown below correspondingly (Figure 8).

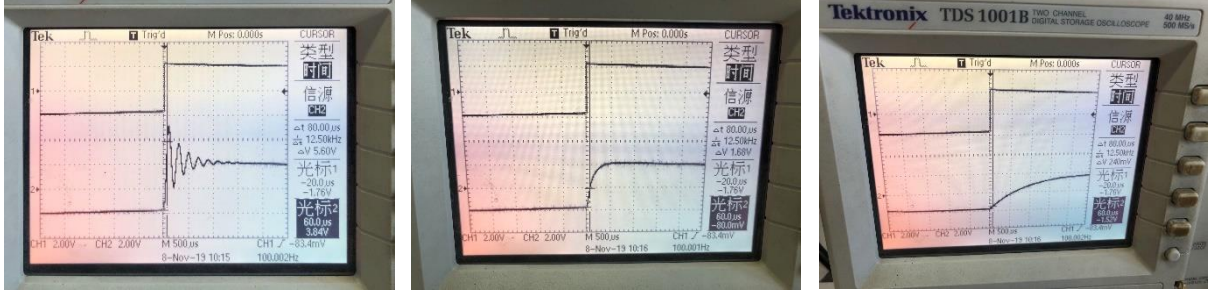


Figure 8. Underdamped, critically damped and overdamped cases for RLC series circuit

Based on the experimental data of $T_{1/2}$, we can calculate the theoretical τ as

$$\tau_{\text{experimental}} = \frac{T_{1/2, \text{experimental}}}{1.68} = 7.1429 \times 10^{-5} \pm 6 \times 10^{-9} [\text{s}].$$

And we can calculate the theoretical value for τ as

$$\tau_{\text{theoretical}} = \sqrt{LC} = \sqrt{0.01 \times 101.21 \times 10^{-9}} = 3.1814 \times 10^{-5} \pm 2 \times 10^{-9} [\text{s}].$$

The relative error between them is

$$\frac{|\tau_{\text{theoretical}} - \tau_{\text{experimental}}|}{\tau_{\text{theoretical}}} \times 100\% = 125\%,$$

which is very large. There may be some wrong operations. For example, we should make the circuit to be critically damped, but this is very hard. The critically damped case only happens when $\beta^2 = \omega_0^2$, which is really difficult to make it, and we may miss it. Besides, the precision of the device may also increase the error. And we do not measure the actual inductance of the inductor and just use the value labeled on it, which will also contribute to the error. Moreover, the inductor is also not ideal. When using the **CURSOR** function, it increases or decreases $10 \mu\text{s}$ each time I adjust it. And I failed to make it more precise. If I can make the device be more precise, for example, increase or decrease $1 \mu\text{s}$ each time, the result will be better.

4.3. RLC resonant circuit

According to the procedure in 3.3., we can get the table below (Table 5).

$R \ 99.64 [\Omega] \pm 0.01 [\Omega], \quad L \ 0.01 [\text{H}] \pm 0 [\text{H}]$		
$C \ 101.21 [\text{nF}] \pm 0.01 [\text{nF}], \quad \varepsilon \ 4.000 [V_{pp}] \pm 0.001 [V_{pp}]$		
	$U_R [V_{pp}] \pm 0.02/0.002 [V_{pp}]$	$f[\text{kHz}] \pm 0.001 [\text{Hz}]$
1	0.304	1.000000
2	0.648	2.000000
3	1.15	3.000000
4	1.74	4.000000
5	3.80	5.000000
6	2.60	6.000000
7	1.68	7.000000
8	1.28	8.000000
9	1.04	9.000000
10	0.880	10.000000
11	0.760	11.000000
12	0.680	12.000000
13	0.640	13.000000
14	0.560	14.000000
15	0.520	15.000000
16	0.480	16.000000
17	0.440	17.000000
18	0.420	18.000000
19	0.392	19.000000
20	0.340	20.000000
21	0.320	21.000000
22	3.24	4.500000
23	2.68	4.200000
24	3.68	4.800000
25	3.64	5.300000
26	3.32	5.500000

Table 5. Measurement data for the U_R vs. f dependence for a RLC resonant circuit

From this table, we can get that

$$U_m = 3.80 [V_{pp}] \pm 0.02 [V_{pp}]$$

$$f_0 = 5.000000 [\text{kHz}] \pm 0.001 [\text{Hz}]$$

In order to get I/I_m , we can calculate U/U_m according to Ohm's law. Taking the first data as an example

$$\frac{I}{I_m} = \frac{U}{U_m} = \frac{0.304}{3.80} = 0.0800 \pm 0.0007$$

$$\frac{f}{f_0} = \frac{1000.000}{5000.000} = 0.2000000 \pm 0.0000002$$

Then, we can get the following table (Table 6).

	$\frac{I}{I_m}$	Uncertainty	$\frac{f}{f_0}$	Uncertainty
1	0.0800	0.0007	0.2000000	0.0000002
2	0.1705	0.0010	0.4000000	0.0000002
3	0.303	0.005	0.6000000	0.0000002
4	0.458	0.006	0.8000000	0.0000003
5	1.000	0.007	1.0000000	0.0000003
6	0.684	0.006	1.2000000	0.0000003
7	0.442	0.006	1.4000000	0.0000003
8	0.337	0.006	1.6000000	0.0000004
9	0.274	0.005	1.8000000	0.0000004
10	0.2316	0.0013	2.0000000	0.0000004
11	0.2000	0.0012	2.2000000	0.0000005
12	0.1789	0.0011	2.4000000	0.0000005
13	0.1684	0.0010	2.6000000	0.0000006
14	0.1474	0.0009	2.8000000	0.0000006
15	0.1368	0.0009	3.0000000	0.0000006
16	0.1263	0.0008	3.2000000	0.0000007
17	0.1158	0.0008	3.4000000	0.0000007
18	0.1105	0.0008	3.6000000	0.0000007
19	0.1032	0.0008	3.8000000	0.0000008
20	0.0895	0.0007	4.0000000	0.0000008
21	0.0842	0.0007	4.2000000	0.0000009
22	0.853	0.007	0.9000000	0.0000003
23	0.705	0.006	0.8400000	0.0000003
24	0.968	0.007	0.9600000	0.0000003
25	0.958	0.007	1.0600000	0.0000003
26	0.874	0.007	1.1000000	0.0000003

Table 6. Calculated value and uncertainty for $\frac{I}{I_m}$ and $\frac{f}{f_0}$

With these data, we can get the figure below (Figure 9).

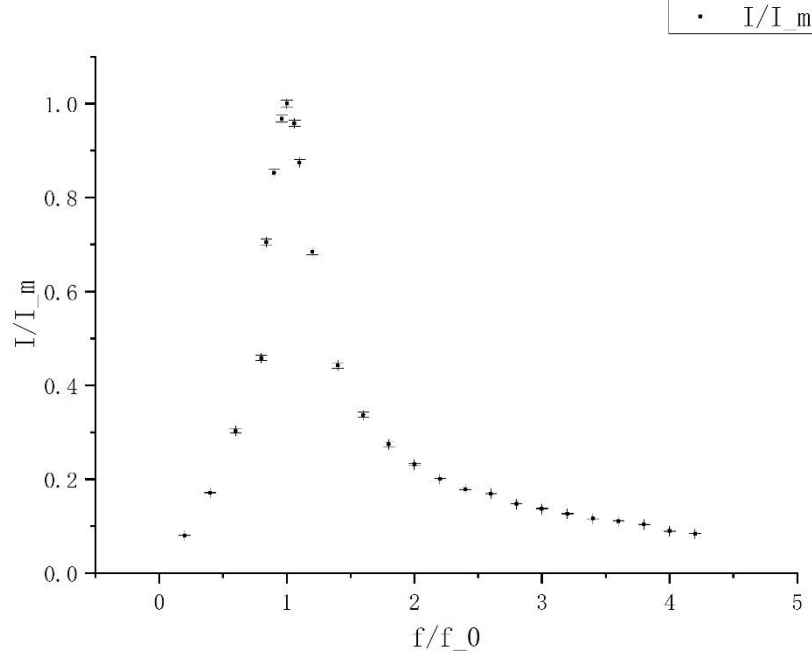


Figure 9. $\frac{I}{I_m}$ vs. $\frac{f}{f_0}$

From this figure, we can find that $\frac{I}{I_m}$ first increases for $\frac{f}{f_0} < 1$. And the increasing speed becomes larger when $\frac{f}{f_0}$ is closer to 1. Then $\frac{I}{I_m}$ reaches a peak at $\frac{f}{f_0} = 1$. Finally, $\frac{I}{I_m}$ decreases for $\frac{f}{f_0} > 1$, and the speed for decreasing becomes slower with the increase of $\frac{f}{f_0}$.

For phase difference, using the first measurement, we can calculate it as:

$$\varphi_{experimental} = \cos^{-1} \frac{U_R}{U_m} = \cos^{-1} \frac{0.304}{3.80} = 1.4907 \pm 0.0007 \text{ [rad]}$$

And we can add the minus sign on $\varphi_{experimental}$ when $\frac{f}{f_0} < 1$. Then, the whole table is listed below (Table 7)

	$\varphi_{experimental}$ [rad]	Uncertainty [rad]	$\frac{f}{f_0}$	Uncertainty
1	-1.4907	0.0007	0.2000000	0.0000002
2	-1.3994	0.0011	0.4000000	0.0000002
3	-1.263	0.006	0.6000000	0.0000002
4	-1.095	0.007	0.8000000	0.0000003
5	0.000	0.000	1.0000000	0.0000003
6	0.817	0.009	1.2000000	0.0000003
7	1.113	0.006	1.4000000	0.0000003
8	1.227	0.006	1.6000000	0.0000004
9	1.294	0.006	1.8000000	0.0000004
10	1.3371	0.0014	2.0000000	0.0000004
11	1.3694	0.0012	2.2000000	0.0000005
12	1.3909	0.0011	2.4000000	0.0000005
13	1.4016	0.0010	2.6000000	0.0000006
14	1.4229	0.0009	2.8000000	0.0000006
15	1.4335	0.0009	3.0000000	0.0000006
16	1.4441	0.0009	3.2000000	0.0000007
17	1.4547	0.0008	3.4000000	0.0000007
18	1.4600	0.0008	3.6000000	0.0000007
19	1.4675	0.0008	3.8000000	0.0000008
20	1.4812	0.0007	4.0000000	0.0000008
21	1.4865	0.0007	4.2000000	0.0000009
22	-0.55	0.01	0.9000000	0.0000003
23	-0.788	0.009	0.8400000	0.0000003
24	-0.25	0.03	0.9600000	0.0000003
25	0.29	0.03	1.0600000	0.0000003
26	0.508	0.014	1.1000000	0.0000003

Table 7. Calculated value and uncertainty for $\varphi_{experimental}$ and $\frac{f}{f_0}$

With these data, we can get the figure below (Figure 10).

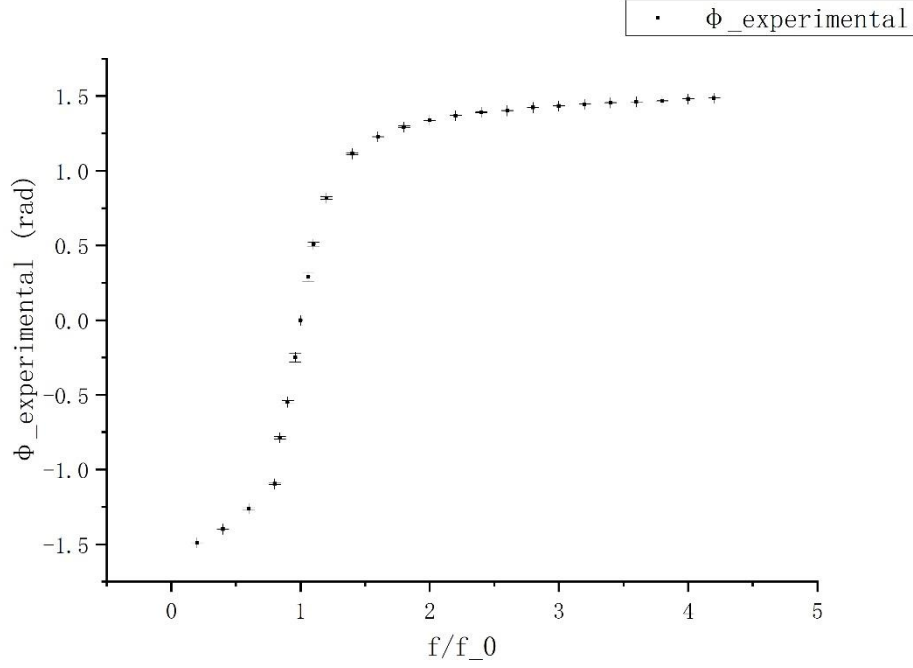


Figure 10. $\phi_{experimental}$ vs. $\frac{f}{f_0}$

From this figure, we can find that the phase difference changes rapidly near $\frac{f}{f_0} = 1$ while the speed of changing slows down when $\frac{f}{f_0}$ is away from 1.

To calculate the theoretical phase difference, we also use the first measurement as an example:

$$\begin{aligned}
 \varphi_{theoretical} &= \tan^{-1} \left(\frac{2\pi f L - \frac{1}{2\pi f C}}{R} \right) \\
 &= \tan^{-1} \left(\frac{2\pi \times 1000.000 \times 0.01 - \frac{1}{2\pi \times 1000.0000 \times 101.21 \times 10^{-9}}}{99.64} \right) \\
 &= -1.504892 \pm 0.000009 \text{ [rad]}
 \end{aligned}$$

The whole table is listed below (Table 8).

	$\varphi_{theoretical}$ [rad]	Uncertainty [rad]	$\frac{f}{f_0}$	Uncertainty
1	-1.504892	0.000009	0.2000000	0.0000002
2	-1.42109	0.00002	0.4000000	0.0000002
3	-1.28225	0.00005	0.6000000	0.0000002
4	-0.95828	0.00014	0.8000000	0.0000003
5	-0.0035	0.0003	1.0000000	0.0000003
6	0.85643	0.00012	1.2000000	0.0000003
7	1.13713	0.00005	1.4000000	0.0000003
8	1.25609	0.00003	1.6000000	0.0000004
9	1.32113	0.00003	1.8000000	0.0000004
10	1.36235	0.00002	2.0000000	0.0000004
11	1.39100	0.00002	2.2000000	0.0000005
12	1.41219	0.00002	2.4000000	0.0000005
13	1.428572	0.000014	2.6000000	0.0000006
14	1.441665	0.000013	2.8000000	0.0000006
15	1.452400	0.000012	3.0000000	0.0000006
16	1.461382	0.000011	3.2000000	0.0000007
17	1.469021	0.000010	3.4000000	0.0000007
18	1.475609	0.000010	3.6000000	0.0000007
19	1.481354	0.000009	3.8000000	0.0000008
20	1.486414	0.000008	4.0000000	0.0000008
21	1.490908	0.000008	4.2000000	0.0000009
22	-0.5899	0.0002	0.9000000	0.0000003
23	-0.8371	0.0002	0.8400000	0.0000003
24	-0.2554	0.0003	0.9600000	0.0000003
25	0.3494	0.0003	1.0600000	0.0000003
26	0.5395	0.0002	1.1000000	0.0000003

Table 7. Calculated value and uncertainty for $\varphi_{theoretical}$ and $\frac{f}{f_0}$

With these data, we can get the figure below (Figure 11).

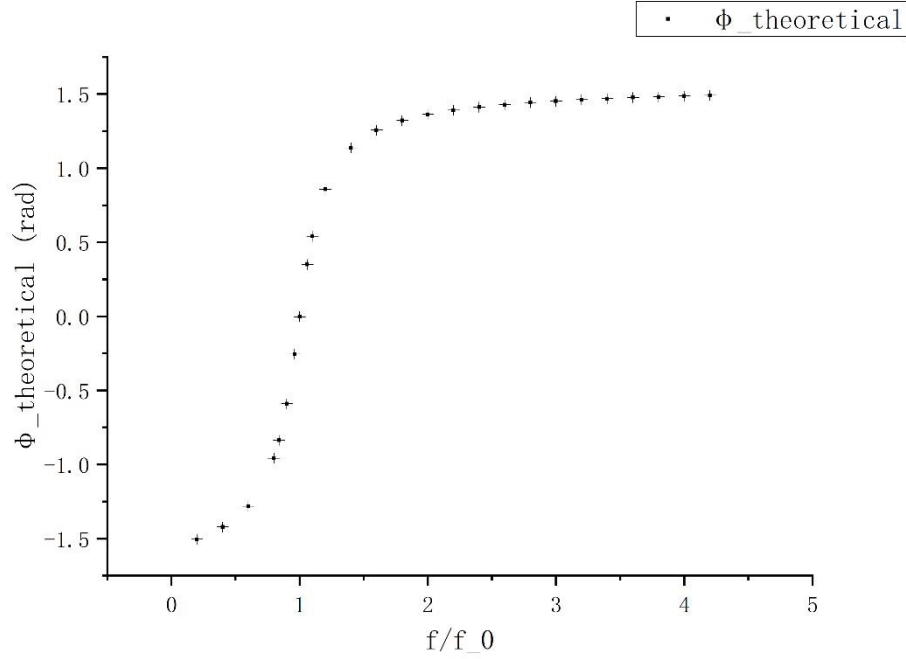


Figure 11. $\phi_{theoretical}$ vs. $\frac{f}{f_0}$

Compared with the experimental one, we can find that they have the same shape. The theoretical resonant frequency can be calculated as

$$f_{theoretical} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.01 \times 101.21 \times 10^{-9}}} = 5002.7 \pm 0.2 \text{ [Hz]},$$

and the relative error is calculated as

$$\frac{|5002.7 - 5000.000|}{5002.7} \times 100\% = 0.06\%,$$

which is very small, and we can assume this part is very successful.

Then, we calculate the quality factor. For the theoretical one,

$$Q_{theoretical} = \frac{\sqrt{LC}}{RC} = \frac{\sqrt{0.01 \times 101.21 \times 10^{-9}}}{99.64 \times 101.21 \times 10^{-9}} = 3.1547 \pm 0.0004$$

For the experimental one,

$$I(f_1) = I(f_2) = \frac{I_m}{\sqrt{2}},$$

then, $f_1 \approx 4200.000 \pm 0.001 \text{ [Hz]}$, $f_2 \approx 6000.000 \pm 0.001 \text{ [Hz]}$

$$Q_{experimental} = \frac{f_0}{f_2 - f_1} = \frac{5000.000}{6000.000 - 4200.000} = 2.777778 \pm 0.000002,$$

and the relative error can be calculated as

$$\frac{|3.1547 - 2.777778|}{3.1547} \times 100\% = 11.95\%,$$

which is relatively large. We may think the reasons for it are that first f_1 and f_2 are found by estimation, which will contribute to the error. Second, the interval between each frequency is large, which prevents us from a more accurate estimation. Third, the points I chose have not covered form an ideal shape in the graph, for example, when $\frac{f}{f_0} < 1$, the dots I have are not enough, which make the graph ends abruptly.

5. Conclusion [1]

5.1. RC, RL series circuit

For RC series circuit, we have

$$\tau_{experimental} = \frac{T_{1/2,experimental}}{\ln 2} = 1.00989 \times 10^{-5} \pm 1.4 \times 10^{-9} [s].$$

$$\tau_{theoretical} = RC = 99.64 \times 101.21 \times 10^{-9} = 1.00846 \times 10^{-5} \pm 1.4 \times 10^{-9} [s].$$

$$\frac{|\tau_{theoretical} - \tau_{experimental}|}{\tau_{theoretical}} \times 100\% = 0.15\%,$$

which is quite successful.

For RL series circuit, we have

$$\tau_{experimental} = \frac{T_{1/2,experimental}}{\ln 2} = 1.154156 \times 10^{-4} \pm 1.4 \times 10^{-9} [s].$$

$$\tau_{theoretical} = \frac{L}{R} = \frac{0.01}{99.64} = 1.004 \times 10^{-4} \pm 1.0 \times 10^{-6} [s].$$

$$\frac{|\tau_{theoretical} - \tau_{experimental}|}{\tau_{theoretical}} \times 100\% = 15.0\%,$$

which is relatively large. We may think that this is mainly because of precision of the device. When using the **CURSOR** function, it increases or decreases $10 \mu s$ each time I adjust it. And I failed to make it more precise. If I can make the device be more precise, for example, increase or decrease $1 \mu s$ each time, the result will be better. Besides, we do not measure the actual inductance of the inductor and just use the value labeled on it, which will also contribute to the error. Besides, the inductor is also not ideal.

5.2. RLC Series Circuit

For RLC series circuit, we have

$$\tau_{experimental} = \frac{T_{1/2,experimental}}{1.68} = 7.1429 \times 10^{-5} \pm 6 \times 10^{-9} [s].$$

$$\tau_{theoretical} = \sqrt{LC} = \sqrt{0.01 \times 101.21 \times 10^{-9}} = 3.1814 \times 10^{-5} \pm 2 \times 10^{-9} [s].$$

$$\frac{|\tau_{theoretical} - \tau_{experimental}|}{\tau_{theoretical}} \times 100\% = 125\%,$$

which is very large. There may be some wrong operations. For example, we should make the circuit to be critically damped, but this is very hard. The critically damped case only happens when $\beta^2 = \omega_0^2$, which is really difficult to make it, and we may miss it. Besides, the precision of the device may also increase the error. And we do not measure the actual inductance of the inductor and just use the value labeled on it, which will also contribute to the error. Moreover, the inductor is also not ideal. When using the **CURSOR** function, it increases or decreases $10 \mu s$ each time I adjust it. And I failed to make it more precise. If I can make the device be more precise, for example, increase or decrease $1 \mu s$ each time, the result will be better.

5.3. RLC Resonant Circuit

In this part, we first have and observe the graph for $\frac{I}{I_m}$ vs. $\frac{f}{f_0}$, and find that $\frac{I}{I_m}$ first increases for $\frac{f}{f_0} < 1$. And the increasing speed becomes larger when $\frac{f}{f_0}$ is closer to 1. Then $\frac{I}{I_m}$ reaches a peak at $\frac{f}{f_0} = 1$. Finally, $\frac{I}{I_m}$ decreases for $\frac{f}{f_0} > 1$, and the speed for decreasing becomes slower with the increase of $\frac{f}{f_0}$.

Then, we calculate $\varphi_{theoretical}$ and $\varphi_{experimental}$, and compare their $\frac{f}{f_0}$ -dependent figures. We find that they have the same shape, so we may think this part is successful.

Then, we calculate theoretical resonant frequency as

$$f_{theoretical} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.01 \times 101.21 \times 10^{-9}}} = 5002.7 \pm 0.2 [Hz],$$

and compare it with the experimental one, and the relative error is 0.06%, which is also quite successful.

Finally, we calculate quality factor theoretically and experimentally,

$$Q_{theoretical} = \frac{\sqrt{LC}}{RC} = \frac{\sqrt{0.01 \times 101.21 \times 10^{-9}}}{99.64 \times 101.21 \times 10^{-9}} = 3.1547 \pm 0.0004$$

$$Q_{experimental} = \frac{f_0}{f_2 - f_1} = \frac{5000.000}{6000.000 - 4200.000} = 2.777778 \pm 0.000002.$$

The relative error is 11.95%, which is relatively large. We may think the reasons for it are that first f_1 and f_2 are found by estimation, which will contribute to the error. Second, the

interval between each frequency is large, which prevents us from a more accurate estimation. Third, the points I chose have not covered form an ideal shape in the graph, for example, when $\frac{f}{f_0} < 1$, the dots I have are not enough, which make the graph ends abruptly.

6. References

- [1] Exercise 5 - lab manual [rev 2.6], UM-JI SJTU. Edited by Qin Tian, Feng Yaming, Gu Yichen, Mateusz Krzyzosiak.
- [2] Uncertainty analysis handbook, UM-JI SJTU.

A. Uncertainty analysis [2]

A.1. Uncertainty for RC , RL series circuit

For both RC and RL series circuit, since $T_{1/2}$ is measured directly, there is only type-B uncertainty:

$$u_{T_{1/2}} = u_B = 0.001 [\mu s]$$

Then, we can calculate the uncertainty for experimental τ as:

$$u_{\tau_{experimental}} = \frac{u_{T_{1/2}}}{\ln 2} = \frac{0.001 \times 10^{-6}}{\ln 2} = 1.4 \times 10^{-9} [s]$$

In RC series circuit, $\tau = RC$. Besides, R and C are measured directly, they only have type-B uncertainty:

$$u_R = u_B = 0.01 [\Omega]$$

$$u_C = u_B = 0.01 \times 10^{-9} = 1 \times 10^{-11} [F]$$

Then, we can calculate the uncertainty for theoretical τ

$$\begin{aligned} u_{\tau_{theoretical}} &= \sqrt{\left(\frac{\partial RC}{\partial R} u_R\right)^2 + \left(\frac{\partial RC}{\partial C} u_C\right)^2} = \sqrt{(C u_R)^2 + (R u_C)^2} \\ &= \sqrt{(101.21 \times 10^{-9} \times 0.01)^2 + (99.64 \times 1 \times 10^{-11})^2} = 1.4 \times 10^{-9} [s] \end{aligned}$$

In RL series circuit, $\tau = \frac{L}{R}$. Besides, R is measured directly, so it only has type-B uncertainty, and we assume the uncertainty for L is 0:

$$u_R = u_B = 0.01 [\Omega]$$

$$u_L = 0 [H]$$

Then, we can calculate the uncertainty for theoretical τ

$$u_{\tau_{theoretical}} = \sqrt{\left(\frac{\partial \frac{L}{R}}{\partial R} u_R\right)^2 + \left(\frac{\partial \frac{L}{R}}{\partial L} u_L\right)^2} = \sqrt{\left(\frac{L u_R}{R^2}\right)^2} = \sqrt{\left(\frac{0.01 \times 0.01}{99.64^2}\right)^2} = 1.0 \times 10^{-6} [s]$$

A.2. Uncertainty for RLC series circuit

For RLC series circuit, since $T_{1/2}$ is measured directly, there is only type-B uncertainty:

$$u_{T_{1/2}} = u_B = 0.01 [\mu s]$$

Then, we can calculate the uncertainty for experimental τ as:

$$u_{\tau_{\text{experimental}}} = \frac{u_{T_{1/2}}}{1.68} = \frac{0.01 \times 10^{-6}}{1.68} = 6 \times 10^{-9} \text{ [s]}$$

In RLC series circuit, $\tau = \sqrt{LC}$. Besides, C is measured directly, so it only has type-B uncertainty, and we assume the uncertainty for L is 0:

$$u_C = u_c = 0.01 \times 10^{-9} = 1 \times 10^{-11} \text{ [F]}$$

$$u_L = 0 \text{ [H]}$$

Then, we can calculate the uncertainty for theoretical τ

$$\begin{aligned} u_{\tau_{\text{theoretical}}} &= \sqrt{\left(\frac{\partial \sqrt{LC}}{\partial C} u_C\right)^2 + \left(\frac{\partial \sqrt{LC}}{\partial L} u_L\right)^2} = \sqrt{\left(\frac{u_C \sqrt{L}}{2\sqrt{C}}\right)^2} \\ &= \sqrt{\left(\frac{1 \times 10^{-11} \times \sqrt{0.01}}{2\sqrt{101.21 \times 10^{-9}}}\right)^2} = 2 \times 10^{-9} \text{ [s]} \end{aligned}$$

A.2. Uncertainty for RLC resonant circuit

Since I, I_m, f and f_0 are measured directly, they only have type-B uncertainty. Besides,

$$\frac{I}{I_m} = \frac{U}{U_m},$$

therefore,

$$u_{\frac{I}{I_m}} = u_{\frac{U}{U_m}}.$$

Then we can get below using the first measurement as an example:

$$\begin{aligned} u_{\frac{I}{I_m}} &= u_{\frac{U}{U_m}} = \sqrt{\left(\frac{\partial \frac{U}{U_m}}{\partial U} \times u_U\right)^2 + \left(\frac{\partial \frac{U}{U_m}}{\partial U_m} \times u_{U_m}\right)^2} = \sqrt{\left(\frac{u_U}{U_m}\right)^2 + \left(\frac{U u_{U_m}}{U_m^2}\right)^2} \\ &= \sqrt{\left(\frac{0.002}{3.80}\right)^2 + \left(\frac{0.304 \times 0.02}{3.80^2}\right)^2} = 0.0007 \\ u_{\frac{f}{f_0}} &= \sqrt{\left(\frac{\partial \frac{f}{f_0}}{\partial f} \times u_f\right)^2 + \left(\frac{\partial \frac{f}{f_0}}{\partial f_0} \times u_{f_0}\right)^2} = \sqrt{\left(\frac{u_f}{f_0}\right)^2 + \left(\frac{f u_{f_0}}{f_0^2}\right)^2} \\ &= \sqrt{\left(\frac{0.001}{5000}\right)^2 + \left(\frac{1000 \times 0.001}{5000^2}\right)^2} = 0.0000002 \end{aligned}$$

The whole table for uncertainty is listed below (Table 8).

	$\frac{I}{I_m}$	Uncertainty	$\frac{f}{f_0}$	Uncertainty
1	0.0800	0.0007	0.2000000	0.0000002
2	0.1705	0.0010	0.4000000	0.0000002
3	0.303	0.005	0.6000000	0.0000002
4	0.458	0.006	0.8000000	0.0000003
5	1.000	0.007	1.0000000	0.0000003
6	0.684	0.006	1.2000000	0.0000003
7	0.442	0.006	1.4000000	0.0000003
8	0.337	0.006	1.6000000	0.0000004
9	0.274	0.005	1.8000000	0.0000004
10	0.2316	0.0013	2.0000000	0.0000004
11	0.2000	0.0012	2.2000000	0.0000005
12	0.1789	0.0011	2.4000000	0.0000005
13	0.1684	0.0010	2.6000000	0.0000006
14	0.1474	0.0009	2.8000000	0.0000006
15	0.1368	0.0009	3.0000000	0.0000006
16	0.1263	0.0008	3.2000000	0.0000007
17	0.1158	0.0008	3.4000000	0.0000007
18	0.1105	0.0008	3.6000000	0.0000007
19	0.1032	0.0008	3.8000000	0.0000008
20	0.0895	0.0007	4.0000000	0.0000008
21	0.0842	0.0007	4.2000000	0.0000009
22	0.853	0.007	0.9000000	0.0000003
23	0.705	0.006	0.8400000	0.0000003
24	0.968	0.007	0.9600000	0.0000003
25	0.958	0.007	1.0600000	0.0000003
26	0.874	0.007	1.1000000	0.0000003

Table 8. Calculated value and uncertainty for $\frac{I}{I_m}$ and $\frac{f}{f_0}$

To calculate the uncertainty for $\varphi = \cos^{-1} \frac{U_R}{U_m}$, using the first measurement as an example:

$$u_\varphi = \sqrt{\left(\frac{\partial \varphi}{\partial U_R} u_{U_R}\right)^2 + \left(\frac{\partial \varphi}{\partial U_m} u_{U_m}\right)^2} = \sqrt{\left(\frac{u_{U_R}}{U_m \sqrt{1 - \left(\frac{U_R}{U_m}\right)^2}}\right)^2 + \left(\frac{U_R u_{U_m}}{U_m^2 \sqrt{1 - \left(\frac{U_R}{U_m}\right)^2}}\right)^2}$$

$$= \sqrt{\left(\frac{0.002}{3.80 \times \sqrt{1 - \left(\frac{0.304}{3.80}\right)^2}}\right)^2 + \left(\frac{0.304 \times 0.02}{3.80^2 \times \sqrt{1 - \left(\frac{0.304}{3.80}\right)^2}}\right)^2} = 0.0007 \text{ [rad]}$$

The whole table for uncertainty is listed below (Table 9).

	$\varphi_{experimental}$ [rad]	Uncertainty [rad]	$\frac{f}{f_0}$	Uncertainty
1	-1.4907	0.0007	0.2000000	0.0000002
2	-1.3994	0.0011	0.4000000	0.0000002
3	-1.263	0.006	0.6000000	0.0000002
4	-1.095	0.007	0.8000000	0.0000003
5	0.000	0.000	1.0000000	0.0000003
6	0.817	0.009	1.2000000	0.0000003
7	1.113	0.006	1.4000000	0.0000003
8	1.227	0.006	1.6000000	0.0000004
9	1.294	0.006	1.8000000	0.0000004
10	1.3371	0.0014	2.0000000	0.0000004
11	1.3694	0.0012	2.2000000	0.0000005
12	1.3909	0.0011	2.4000000	0.0000005
13	1.4016	0.0010	2.6000000	0.0000006
14	1.4229	0.0009	2.8000000	0.0000006
15	1.4335	0.0009	3.0000000	0.0000006
16	1.4441	0.0009	3.2000000	0.0000007
17	1.4547	0.0008	3.4000000	0.0000007
18	1.4600	0.0008	3.6000000	0.0000007
19	1.4675	0.0008	3.8000000	0.0000008
20	1.4812	0.0007	4.0000000	0.0000008
21	1.4865	0.0007	4.2000000	0.0000009
22	-0.55	0.01	0.9000000	0.0000003
23	-0.788	0.009	0.8400000	0.0000003
24	-0.25	0.03	0.9600000	0.0000003
25	0.29	0.03	1.0600000	0.0000003
26	0.508	0.014	1.1000000	0.0000003

Table 9. Calculated value and uncertainty for $\varphi_{experimental}$ and $\frac{f}{f_0}$

To calculate the uncertainty for $\varphi = \tan^{-1}\left(\frac{2\pi fL - \frac{1}{2\pi fC}}{R}\right)$, using the first measurement as an

example:

$$\begin{aligned}
u_\varphi &= \sqrt{\left(\frac{\partial\varphi}{\partial f}u_f\right)^2 + \left(\frac{\partial\varphi}{\partial C}u_C\right)^2 + \left(\frac{\partial\varphi}{\partial R}u_R\right)^2} \\
&= \sqrt{\left(\frac{u_f R \left(2\pi L + \frac{1}{2\pi f^2 C}\right)}{R^2 + \left(2\pi f L - \frac{1}{2\pi f C}\right)^2}\right)^2 + \left(\frac{u_C R \times \frac{1}{2\pi f C^2}}{R^2 + \left(2\pi f L - \frac{1}{2\pi f C}\right)^2}\right)^2 + \left(\frac{u_R \left(\frac{1}{2\pi f C} - 2\pi f L\right)}{R^2 + \left(2\pi f L - \frac{1}{2\pi f C}\right)^2}\right)^2} \\
\frac{u_f R \left(2\pi L + \frac{1}{2\pi f^2 C}\right)}{R^2 + \left(2\pi f L - \frac{1}{2\pi f C}\right)^2} &= \frac{0.001 \times 99.64 \times \left(2\pi \times 0.01 + \frac{1}{2\pi \times 1000^2 \times 101.21 \times 10^{-9}}\right)}{99.64^2 + \left(2\pi \times 1000 \times 0.01 - \frac{1}{2\pi \times 1000 \times 101.21 \times 10^{-9}}\right)^2} \\
&= 7.12 \times 10^{-8} \\
\frac{u_C R \times \frac{1}{2\pi f C^2}}{R^2 + \left(2\pi f L - \frac{1}{2\pi f C}\right)^2} &= \frac{0.01 \times 10^{-9} \times 99.64 \times \frac{1}{2\pi \times 1000 \times (101.21 \times 10^{-9})^2}}{99.64^2 + \left(2\pi \times 1000 \times 0.01 - \frac{1}{2\pi \times 1000 \times 101.21 \times 10^{-9}}\right)^2} \\
&= 6.76 \times 10^{-6} \\
\frac{u_R \left(\frac{1}{2\pi f C} - 2\pi f L\right)}{R^2 + \left(2\pi f L - \frac{1}{2\pi f C}\right)^2} &= \frac{0.01 \times \left(\frac{1}{2\pi \times 1000 \times 101.21 \times 10^{-9}} - 2\pi \times 1000 \times 0.01\right)}{99.64^2 + \left(2\pi \times 1000 \times 0.01 - \frac{1}{2\pi \times 1000 \times 101.21 \times 10^{-9}}\right)^2} \\
&= 6.60 \times 10^{-6} \\
u_\varphi &= \sqrt{(7.12 \times 10^{-8})^2 + (6.76 \times 10^{-6})^2 + (6.60 \times 10^{-6})^2} = 9 \times 10^{-6} \text{ [rad]}
\end{aligned}$$

The whole table for uncertainty is listed below (Table 10).

	$\varphi_{theoretical}$ [rad]	Uncertainty [rad]	$\frac{f}{f_0}$	Uncertainty
1	-1.504892	0.000009	0.2000000	0.0000002
2	-1.42109	0.00002	0.4000000	0.0000002
3	-1.28225	0.00005	0.6000000	0.0000002
4	-0.95828	0.00014	0.8000000	0.0000003
5	-0.0035	0.0003	1.0000000	0.0000003
6	0.85643	0.00012	1.2000000	0.0000003
7	1.13713	0.00005	1.4000000	0.0000003
8	1.25609	0.00003	1.6000000	0.0000004
9	1.32113	0.00003	1.8000000	0.0000004
10	1.36235	0.00002	2.0000000	0.0000004
11	1.39100	0.00002	2.2000000	0.0000005
12	1.41219	0.00002	2.4000000	0.0000005
13	1.428572	0.000014	2.6000000	0.0000006
14	1.441665	0.000013	2.8000000	0.0000006
15	1.452400	0.000012	3.0000000	0.0000006
16	1.461382	0.000011	3.2000000	0.0000007
17	1.469021	0.000010	3.4000000	0.0000007
18	1.475609	0.000010	3.6000000	0.0000007
19	1.481354	0.000009	3.8000000	0.0000008
20	1.486414	0.000008	4.0000000	0.0000008
21	1.490908	0.000008	4.2000000	0.0000009
22	-0.5899	0.0002	0.9000000	0.0000003
23	-0.8371	0.0002	0.8400000	0.0000003
24	-0.2554	0.0003	0.9600000	0.0000003
25	0.3494	0.0003	1.0600000	0.0000003
26	0.5395	0.0002	1.1000000	0.0000003

Table 10. Calculated value and uncertainty for $\varphi_{theoretical}$ and $\frac{f}{f_0}$

In order to calculate the uncertainty for theoretical resonant frequency, we can calculate as below. Since $f_{theoretical} = \frac{1}{2\pi\sqrt{LC}}$, then

$$\begin{aligned}
u_{f_{theoretical}} &= \sqrt{\left(\frac{\partial f_{theoretical}}{\partial L} u_L\right)^2 + \left(\frac{\partial f_{theoretical}}{\partial C} u_C\right)^2} = \sqrt{\left(\frac{u_L}{4\pi L\sqrt{LC}}\right)^2 + \left(\frac{u_C}{4\pi C\sqrt{LC}}\right)^2} \\
&= \sqrt{\left(\frac{0.01 \times 10^{-9}}{4\pi \times 101.21 \times 10^{-9} \times \sqrt{0.01 \times 101.21 \times 10^{-9}}}\right)^2} = 0.2 \text{ [Hz]}
\end{aligned}$$

Since $Q_{theoretical} = \frac{\sqrt{LC}}{RC}$, then we can calculate the uncertainty as follows.,

$$\begin{aligned}
u_{Q_{theoretical}} &= \sqrt{\left(\frac{\partial Q_{theoretical}}{\partial L} u_L\right)^2 + \left(\frac{\partial Q_{theoretical}}{\partial C} u_C\right)^2 + \left(\frac{\partial Q_{theoretical}}{\partial R} u_R\right)^2} \\
&= \sqrt{\left(\frac{\sqrt{L}}{2RC\sqrt{C}} u_C\right)^2 + \left(\frac{\sqrt{L}}{R^2\sqrt{C}} u_R\right)^2} \\
&= \sqrt{\left(\frac{\sqrt{0.01} \times 0.01 \times 10^{-9}}{2 \times 99.64 \times 101.21 \times 10^{-9} \times \sqrt{101.21 \times 10^{-9}}}\right)^2 + \left(\frac{\sqrt{0.01} \times 0.01}{99.64^2 \sqrt{101.21 \times 10^{-9}}}\right)^2} \\
&= 0.0004
\end{aligned}$$

Since $Q_{experimental} = \frac{f_0}{f_2 - f_1}$, then we can calculate the uncertainty as follows,

$$\begin{aligned}
u_{Q_{experimental}} &= \sqrt{\left(\frac{\partial Q_{experimental}}{\partial f_0} u_{f_0}\right)^2 + \left(\frac{\partial Q_{experimental}}{\partial f_2} u_{f_2}\right)^2 + \left(\frac{\partial Q_{experimental}}{\partial f_1} u_{f_1}\right)^2} \\
&= \sqrt{\left(\frac{u_{f_0}}{f_2 - f_1}\right)^2 + \left(\frac{f_0 \times u_{f_2}}{(f_2 - f_1)^2}\right)^2 + \left(\frac{f_0 \times u_{f_1}}{(f_2 - f_1)^2}\right)^2} \\
&= \sqrt{\left(\frac{0.001}{6000 - 4200}\right)^2 + \left(\frac{5000 \times 0.001}{(6000 - 4200)^2}\right)^2 + \left(\frac{5000 \times 0.001}{(6000 - 4200)^2}\right)^2} \\
&= 0.000002
\end{aligned}$$