

UM-SJTU PHYSICS LABORATORY VP241
DATA SHEET (EXERCISE 5)

Name: 周雅宁

Student ID: 518021911039

Group: 8

Date: 11.8

NOTICE. Please remember to show the data sheet to your instructor before leaving the laboratory. The data sheet will not be accepted if the data are recorded with pencil or modified by correction fluid/tape. If a mistake is made in recording a datum item, cancel the wrong value by drawing a fine line through it, record the correct value legibly, and ask your instructor to confirm the correction. Please remember to take a record of the precision of the instruments used. You are required to hand in the original data with your lab report, so please keep the data sheet properly.

R	$99.64 \Omega \pm 0.01 \Omega$	f	$5.0000 \text{ kHz} \pm 0.001 \text{ Hz}$	\mathcal{E}	$4.000 \text{ Vpp} \pm 0.001 \text{ Vpp}$
C	$101.2 \text{ nF} \pm 0.01 \text{ nF}$	$T_{1/2}$	$7.000 \text{ } \mu\text{s} \pm 0.001 \text{ } \mu\text{s}$		


Table 1. $T_{1/2}$ measurement data for a RC series circuit.

R	$99.64 \Omega \pm 0.01 \Omega$	f	$1.0000 \text{ kHz} \pm 0.001 \text{ Hz}$	\mathcal{E}	$4.00 \text{ Vpp} \pm 0.001 \text{ Vpp}$
L	$2.01 \text{ H} \pm 0.01 \text{ H}$	$T_{1/2}$	$80.00 \text{ } \mu\text{s} \pm 0.01 \text{ } \mu\text{s}$		

Table 2. $T_{1/2}$ measurement data for a RL series circuit.

L	$0.01 \text{ H} \pm 0.001 \text{ H}$	C	$101.2 \text{ nF} \pm 0.01 \text{ nF}$	\mathcal{E}	$4.000 \text{ Vpp} \pm 0.001 \text{ Vpp}$	f	$100.0000 \text{ kHz} \pm 0.001 \text{ Hz}$
βt	1.68	$T_{1/2}$	$120.00 \text{ } \mu\text{s} \pm 0.01 \text{ } \mu\text{s}$				

Table 3. $T_{1/2}$ measurement data for a critically damped RLC series circuit.

Instructor's signature: 

R $99.6 \Omega \pm 0.01 \Omega$		L $1.0 \text{ mH} \pm 0.1 \text{ mH}$		C $10.2 \text{ nF} \pm 0.01 \text{ nF}$	
f_0 $5.000 \text{ kHz} \pm 0.001 \text{ kHz}$		ϵ $4.000 \text{ Vpp} \pm 0.001 \text{ Vpp}$		V_{pp}	
U_R	$V_{pp} \pm 0.001 \text{ Vpp}$	V_{pp}	f $\text{kHz} \pm 0.001 \text{ kHz}$	H_z	
1	1.20	0.304	3.000000	1.000000	
2	3.80	0.648	5.000000	2.000000	
3	1.72	1.15	7.000000	3.000000	
4	1.04	1.74	9.000000	4.000000	
5	0.760	3.80	11.000000	5.000000	
6	0.600	2.60	13.000000	6.000000	
7	0.480	1.68	15.000000	7.000000	
8	0.432	1.28	17.000000	8.000000	
9	0.392	1.04	19.000000	9.000000	
10	0.336	0.880	21.000000	10.000000	
11		0.760		11.000000	
12		0.680		12.060000	
13		0.640		13.000000	
14		0.560		14.000000	
15		0.520		15.000000	
16		0.480		16.000000	
17		0.440		17.000000	
18		0.420		18.000000	
19		0.392		19.000000	
20		0.340		20.000000	
21		0.320		21.000000	

Table 4. Measurement data for the U_R vs. f dependence for a RLC resonant circuit.

3.74

2.68

3.68

3.64

3.32

4.500000

4.200000

4.800000

5.300000

5.500000

Instructor's signature: _____